

Lab Results

Case-A: Data for charging a single capacitor

Table-1 Resistance R = 100 Capacitance C = 0.05

Time s	Measured Voltage v	Charge on Capacitor
0.50	0.30	0.015
1.00	0.85	0.042
1.50	1.20	0.06
2.00	1.80	0.09
2.50	2.30	0.115
3.00	2.90	0.145
3.05	3.50	0.175
4.00	4.77	0.238
4.05	5.32	0.266
5.00	5.89	0.295
7.00	6.13	0.307
10.0	6.50	0.325
15.0	7.90	0.395
20.0	8.33	0.417
25.0	9.20	0.46

Table 2 Maximum Charge from eqn (2) = $Q = \underline{0.46}$ RC time constant from

eqn (3) = $\tau = \underline{15}$

	Calculated value eqn (1)	Experimental value eqn (5)	% error
Charge at $t = 1 \tau$	0.46	0.39	6
Charge at $t = 2 \tau$	1.2	1.2	0
Charge at $t = 3 \tau$	3.2	2.6	43.75

Case C and D: Data for Two Capacitors in Series and Parallel: Table 5: Resistance:

$\underline{100}$ Capacitance 1: $\underline{0.05}$ Capacitance 2:

$\underline{0.10}$

Type of Circuit Capacitors in:	Calculated values of τ_C and τ_D	Measured Charging time τ_C	Measured Discharging time τ_D	Percent error in time of charging	Percent error in time of discharging
Series	300	13	14	7.69	15.38
Parallel	1.5	8	6	25	37.5