

Project 7

Design a synchronous sequential circuit that steps through the sequence

1 – 3 – 5 – 7 – 4 – 2 – 0 – 6

and repeats.

Implement the circuit in Verilog. Drive the 7-segment display with the circuit assigned above. Demonstrate the circuit, and turn in your Verilog and Constraints files.