

Physics Homework.

1. $Q = CV$

$$V_1 = \frac{Q_1}{C_1} = \frac{8.3 \times 10^{-6}}{5.6 \times 10^{-6}}$$

$$V_1 = 1.482 \text{ V}$$

2. $W_2 = 4.3 \times 10^{-6}$

But, $W = \frac{1}{2} C_2 V_2^2 = 4.3 \times 10^{-6}$

$$V_2 = 2.48 \text{ V}$$

3. $Q_2 + Q_3 = Q_1$

$$C_2 V_2 + C_3 V_3 = C_1 V_1$$

$$V_3 = \frac{Q}{C} = \frac{4.828}{1.4}$$

$$V_3 = 3.45 \text{ V}$$

4. $Q_2 + Q_3 = Q_1$

$$Q_3 = Q_1 - Q_2 = (8.3 - 3.472) \times 10^{-6}$$

$$Q_3 = 4.828 \times 10^{-6} \text{ C}$$

5. For Series Connection.

Equivalent Capacitance, C_T

$$C_T = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} + \frac{1}{C_5}}$$

$$= \frac{1}{\frac{1}{0.7} + \frac{1}{1.9} + \frac{1}{3.8} + \frac{1}{6.4} + \frac{1}{6.4}}$$

$$= 0.395 \times 10^{-6} \text{ F}$$

6. $V = 7 \text{ V}$

$$C = 3.8 \times 10^{-6} \text{ F}$$

Charge $Q = CV$

$$= 7 \times 3.8 \times 10^{-6}$$

$$= 26.6 \times 10^{-6} \text{ C}$$

7. $C = 3.8 \times 10^{-6} \text{ F}$

Given $Q = 26.6 \times 10^{-6}$

Then $V = \frac{Q}{C} = \frac{26.6 \times 10^{-6}}{3.8 \times 10^{-6}}$

$$= 7 \text{ V}$$

8. Energy = $\frac{1}{2} CV^2$

$$= \frac{1}{2} 3.8 \times 10^{-6} \times 7^2$$

$$= 93.1 \times 10^{-6} \text{ J}$$

9. Capacitors in Parallel:

Equivalent Capacitance, $C_T =$

$$C_T = C_1 + C_2 + C_3 + \dots + C_n$$

$$= (0.7 + 1.9 + 3.8 + 6.4 + 6.4) \times 10^{-6}$$

$$= 19.2 \times 10^{-6} \text{ F}$$

$$10 \quad C = 3.8 \times 10^{-6} \text{ F}$$

$$V = 7 \text{ V}$$

$$Q = CV$$

$$= (3.8 \times 7) \times 10^{-6} \text{ C}$$

$$= 26.6 \times 10^{-6} \text{ C}$$

$$11. \quad P.D = V$$

$$V = \frac{Q}{C} = \frac{26.6 \times 10^{-6} \text{ C}}{4.0 \times 10^{-6} \text{ F}}$$

$$= 6.65 \text{ V}$$

$$12. \quad E = W = \frac{1}{2} CV^2$$

$$C = 19.2 \times 10^{-6} \text{ F}$$

$$V = 6.65 \text{ V}$$

$$= \frac{1}{2} 19.2 \times 10^{-6} \times 6.65^2$$

$$= 424.5 \times 10^{-6} \text{ J}$$

$$13. \quad R_E = R_1 + R_2$$

$$= (7 + 11.4) = 18.4 \text{ } \Omega$$

$$14. \quad R_E^{-1} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{7} + \frac{1}{11.4}$$

$$R_E = \frac{1}{0.23}$$

$$= \underline{\underline{4.34 \text{ } \Omega}}$$

$$15. \quad R_E = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$= 4.34 + 4.34$$

$$= \underline{\underline{8.67 \text{ } \Omega}}$$

$$16. \quad R_E = R_1 + R_2 = 18.4 \text{ } \Omega$$

$$V = 4.6 \text{ V}$$

$$\text{Current } I = \frac{V}{R} = \frac{4.6}{18.4}$$

$$= \underline{\underline{0.25 \text{ A}}}$$

$$17. \quad P_{\text{out}} = \frac{V^2}{R_E} = \frac{4.6^2}{18.4}$$

$$= 1.15 \text{ W}$$

$$18. \quad P_{R_1} = \frac{V^2}{R_1} = \frac{4.6^2}{7}$$

$$= 3.02 \text{ W}$$

$$19. \quad P_{R_2} = \frac{V^2}{R_2} = \frac{4.6^2}{11.4}$$


$$= 1.86 \text{ W}$$

20. $I = \frac{V}{R}$

$$I_{R_1} = \frac{R_1}{R_1 + R_3} I_s \quad I = \frac{4V}{2\Omega} = 2A$$

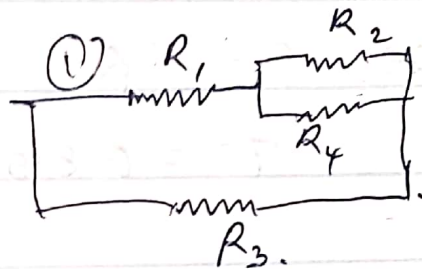21. $R_{Tot} \Rightarrow$

$$\frac{1}{R_{Tot}} = \frac{1}{R_3} + \frac{1}{R_1 + R_4}$$



$$\textcircled{1} \cdot \left(\frac{1}{R_2 + R_4} \right)^{-1} + R_1 + \dots$$

$$= 3.43 + 2 = 5.43 \Omega$$

$$= R_3 = 12 \Omega$$

$$\frac{1}{R_{Tot}} = \frac{1}{5.43} + \frac{1}{12}$$

$$= \underline{\underline{3.74 \Omega}}$$

22. $I = \frac{V}{R} = \frac{4}{3.74} = 1.07A$
 $= \underline{\underline{1.07A}}$

23. $I_{R_2} = \frac{R_2}{R_1 + R_3} I = 0.459A$

$$24. P = \frac{V^2}{R} = IV$$

$$I = \frac{P}{V} = \frac{75W}{92V} = 0.815 A$$

$$25. P = I^2 R$$

$$75 = 0.815^2 R$$

$$R = 112.9 \Omega$$

$$26. R = \frac{R_1}{2} = \frac{112.9}{2} = 56.45 \Omega.$$

$$V = 92V.$$

$$P = \frac{V^2}{R} = \frac{92^2}{56.45}$$

$$= 149.9 W$$

$$\approx 150 W$$

27. The higher the Power, the lower the resistance.

$$28. I_1 = \frac{V_1}{R_1} = \frac{8V}{110\Omega} = 0.0727 A$$

$$29. I_3 = I_1 + I_2$$

$$I_2 = \frac{5}{80} = 0.0625$$

$$I_3 = 0.135 A$$

$$30. Q = CV$$

$$= 135 \times 10^{-6} \times 9 \text{ V}$$

$$= 1215 \times 10^{-6} \text{ C}$$

$$I = \frac{V}{R} = \frac{9}{55000} = 163.6 \times 10^{-6} \text{ A.}$$

$$I = \frac{Q}{T}$$

$$T = \frac{Q}{I} = \frac{1215 \times 10^{-6}}{163.6 \times 10^{-6}} = \underline{\underline{7.43 \text{ s}}} \text{ for } 9 \text{ V.}$$

$$T = \frac{675}{163.6} = \underline{\underline{4.13 \text{ s}}} \text{ for } 5 \text{ V}$$

$$31. V_c = \frac{Q}{C} = 9 \text{ V}$$

$$32. Q = CV = 135 \times 10^{-6} \times 9$$

$$= \underline{\underline{1215 \times 10^{-6} \text{ C.}}}$$

$$33. E_c = \frac{1}{2} CV^2 = \frac{1}{2} (135 \times 10^{-6}) \times 9^2$$

$$= \underline{\underline{54.67 \times 10^{-4} \text{ J}}}$$

$$34. T = 3.2 \text{ } \mu\text{Sec.}$$

$$= 3.2 \times 10^{-6} \text{ s}$$

$$P_B = \left(\frac{Q}{t} \right) V = \frac{1215 \times 10^{-6}}{3.2 \times 10^{-6}} \times 9$$

$$= \underline{\underline{3417.19 \text{ W}}}$$