

①

$$Q_1 = 8.3 \times 10^{-6} \text{ C}$$

$$C_1 = 5.6 \times 10^{-6} \text{ F}$$

$$C_2 = 1.4 \times 10^{-6} \text{ F}$$

Energy stored on C_2 is $U_2 = 4.3 \times 10^{-6} \text{ J}$

Potential diff. C_1

$$Q_1 = V_1 C_1 \quad V_1 = Q_1 / C_1$$

$$V_1 = \frac{8.3 \times 10^{-6}}{5.6 \times 10^{-6}} = \underline{1.4821 \text{ V}} \approx \underline{1.48 \text{ V}}$$

②

$$V_2 = \sqrt{Q_2 / C_2} = \left(\sqrt{2 \cdot Q_2 / 1.4 \times 10^{-6}} \right) = \underline{1.48 \text{ V}}$$

$$= \sqrt{\frac{(2 \times 4.3 \times 10^{-6})}{1.4 \times 10^{-6}}} = 2.4785 \approx \underline{2.48 \text{ V}}$$

$$= 2.48 \text{ V}$$

Since C_2 and C_3 are in parallel.

③

$$V_3 = V_2 = 2.48 \text{ V}$$

$$\underline{V_3 = 2.48 \text{ V}} = \underline{2.48 \text{ V}}$$

④

$$Q_3 = Q_1 - Q_2$$

$$Q_2 = C_2 V_2$$

$$1.4 \times 10^{-6} \times 2.48 = 3.472 \times 10^{-6}$$

$$Q_2 = 3.47 \times 10^{-6}$$

$$Q_3 = 8.3 \times 10^{-6} - 3.47 \times 10^{-6}$$

$$= \underline{4.83 \times 10^{-6} \text{ C}}$$

$$= \underline{4.83 \times 10^{-6} \text{ C}}$$

$$Q5 \quad \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} + \frac{1}{C_5}$$

$$\frac{1}{C} = \frac{1}{0.7 \times 10^{-6}} + \frac{1}{1.4 \times 10^{-6}} + \frac{1}{3.8 \times 10^{-6}} + \frac{1}{6.4 \times 10^{-6}} + \frac{1}{6.4 \times 10^{-6}}$$

$$= 2.53 \times 10^6$$

$$C = \frac{1}{2.53 \times 10^6} = \underline{\underline{0.395 \times 10^{-6} \text{ F}}} \Rightarrow \underline{\underline{0.395 \times 10^{-6} \text{ F}}}$$

$$Q6 \quad Q = ? \quad V = 7V$$

$$Q = CV = 0.395 \times 10^{-6} \times 7 = 2.765 \times 10^{-6} \text{ C}$$

$$= \underline{\underline{2.765 \times 10^{-6} \text{ C}}} \approx \underline{\underline{2.765 \times 10^{-6} \text{ C}}}$$

$$Q7 \quad V = ? \quad \frac{Q}{C_3} = \frac{2.765 \times 10^{-6}}{3.8 \times 10^{-6}} = 0.7276V$$

$$= \underline{\underline{0.7276V}}$$

$$\underline{\underline{0.7276V}}$$

$$Q_8 \quad \text{Energy} = \frac{1}{2} C v^2$$

$$= \frac{1}{2} \times 0.395 \times 10^{-6} \times 7^2$$

$$\underline{\underline{9.6775 \times 10^{-6} \text{ J}}}$$

$$\underline{\underline{9.6775 \times 10^{-6} \text{ J}}}$$

$$Q_9 \quad \text{Capacitors parallel. } C = C_1 + C_2 + C_3 + C_4 + C_5$$

$$0.7 \times 10^{-6} + 1.9 \times 10^{-6} + 3.8 \times 10^{-6} + 6.4 \times 10^{-6} + 6.2 \times 10^{-6}$$

$$= \underline{\underline{19.2 \times 10^{-6} \text{ F}}} = \underline{\underline{19.2 \times 10^{-6} \text{ F}}}$$

Q₁₀

$$V = 7V$$

$$3.8 \times 10^{-6} \times 7 = \underline{\underline{26.6 \times 10^{-6} \text{ C}}} \Rightarrow \underline{\underline{26.6 \times 10^{-6} \text{ C}}}$$

Q11

$$4.0 \times 10^{-6} \text{ F}$$

$$V = \underline{7V} \Rightarrow \underline{7V}$$

$$\underline{Q_{12}} = \frac{1}{2} C V^2$$

$$= \frac{1}{2} \times 4.0 \times 10^{-6} \times 7^2$$

$$= \cancel{470.4} \times 10^{-6} \text{ J}$$

$$= \underline{470.4 \times 10^{-6} \text{ J}} \Rightarrow \underline{470.4 \times 10^{-6} \text{ J}}$$

$$Q_{13} R = R_1 + R_2$$

$$= 7 + 11.4 = \underline{18.4 \Omega} \Rightarrow \underline{18.4 \Omega}$$

$$Q_{14} R_e^{-1} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{7} + \frac{1}{11.4} = \frac{1}{6.23}$$

$$= \underline{6.23 \Omega} = 4.34 \Omega$$

Q15

$$R_{12} = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{11.4 \times 7}{11.4 + 7} = \frac{79.8}{18.4}$$

$$R_1 = 7, R_2 = 3.5$$

$$= \frac{24.537 + 3.5}{10.4} = \underline{7.84 \Omega}$$

Q₁₆

$$V = 4.6V$$

$$I = \frac{V}{R} = \frac{4.6}{18.4} = 0.25A$$

Q₁₇

$$\frac{V^2}{R} = \frac{4.6^2}{18.4} = 1.15W$$

Q₁₈

$$P_{R_1} = I^2 R_1 = (0.25)^2 \times 7 = 0.4375W$$

Q₁₉

$$P_{R_2} = I^2 R_2 = (0.25)^2 \times 11.4 = 0.7125W$$

Q₂₀

$$I = \frac{4V}{2\Omega} = 2A$$

13

Q₂₁

$$R_{tot} = ?$$

$$R_2 \text{ and } R_4 = \frac{R_2 \times R_4}{R_2 + R_4} = \frac{6 \times 3}{14} = \frac{24}{7} \Omega$$

$$R_{243} = \frac{24}{7} + \frac{12}{1} = \frac{24 + 84}{7}$$

$$R_{243} = \frac{108}{7}$$

$$R_{eq} = \frac{108/7 \times 2}{108/7 + 2} = \underline{\underline{1.7705 \Omega}}$$

$$= 1.7705 \Omega$$

Q₂₂

Current supplied by battery

$$= \frac{4}{1.7705} = 2.2592$$

$$= 2.2592 A$$

$$\Rightarrow \underline{\underline{2.2592 A}}$$

Q₂₃R₂?

$$\frac{V_{24}}{R_2} = \frac{0.95}{16} = \underline{\underline{0.16 A}}$$

$$\underline{\underline{= 0.16 A}}$$

Q24

$$I = P_v = 75 / 92 = 0.815 \text{ A}$$

Q25

$$75 = I^2 R$$

$$R = 92 / 0.815^2$$

$$= 112.9 \Omega$$

$$= 112.98 \Omega \approx 112.88 \Omega$$

Q26

$$R/2 = 112.98 / 2 = 56.49$$

$$= 92^2 / 56.49 = 149.93 \text{ W}$$

$$= 149.93 \text{ W}$$

$$\approx 149.9 \text{ W} = 149.96 \text{ W}$$

Q27

The higher the power, the lower the resistance

Q₂₈

$$R_1 = 10 \quad R_2 = 40 \quad R_3 = 40 \quad R_4 = 50$$

$$\underline{I_1 = 0.031 A}$$

Q₂₉

$$\underline{I_2 = 0.08 A}$$

Q₃₀

$$R = 55 k\Omega$$

$$V = 9V$$

$$C = 135 \mu F$$

$$5V?$$

$$\underline{T_1 = 6.02 \text{ sec}}$$

Q₃₁

$$\underline{V = 9 V}$$

Q₃₂

$$135 \times 9 = \underline{1215 \mu C}$$

Q₃₃

$$\frac{1}{2} \times 135 \times 10^{-6} = \underline{5.47 \times 10^{-3} J}$$

Q₃₄

$$\frac{5.47 \times 10^{-3}}{3.2 \times 10^{-6}} = \underline{\underline{1709.375}}$$